

國立勤益科技大學九十六學年度研究所碩士班招生筆試試題卷

所別：電子工程系碩士班

組別：電子組

科目：電子學

准考證號碼：□□□□□□□□ (考生自填)

考生注意事項：

- 一、考試時間 100 分鐘。
- 二、共 3 頁考題，可使用計算機。

試題一：〈20 分〉

For the circuit shown in Fig. 1 first, evaluate $T_i(s) = V_i(s)/V_s(s)$ and the corresponding cutoff (corner) frequency. Second, evaluate $T_o(s) = V_o(s)/V_i(s)$ and the corresponding cutoff frequency.

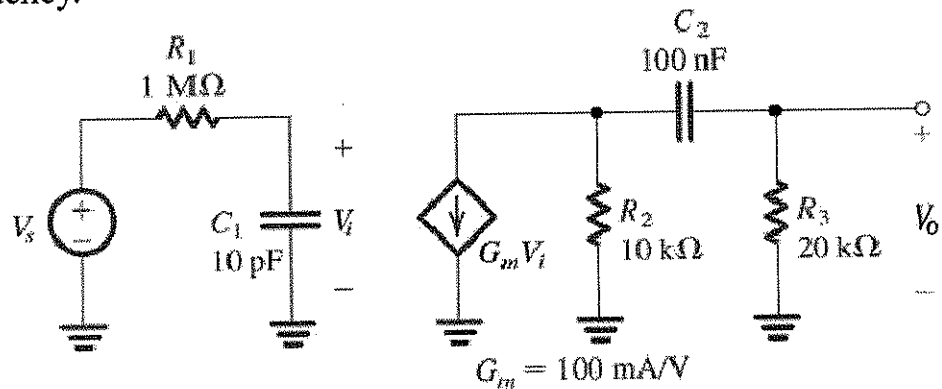


Fig. 1

試題二：〈10 分〉

Assuming the op amp to be ideal, derive an expression for the closed-loop gain v_o/v_i of the circuit shown in Fig. 2.

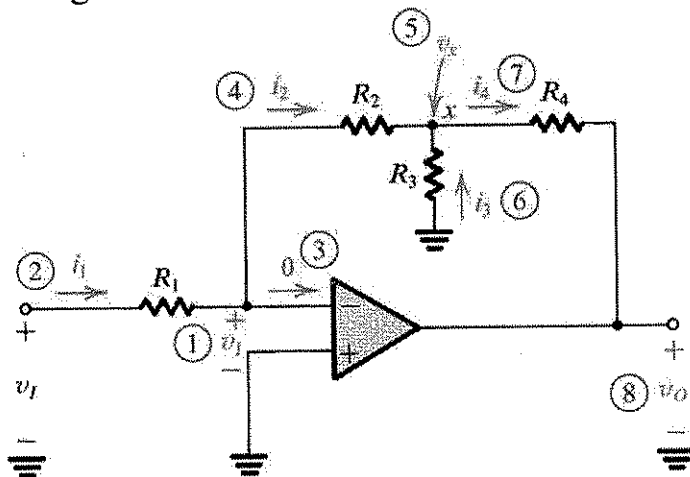


Fig. 2

試題三：〈10分〉

The 6.8-V zener diode in the circuit of Fig. 3 is specified to have $V_z=6.8$ V at $I_z=5$ mA, $r_z=20$ Ω , and $I_{ZK}=0.2$ mA. The supply voltage V^+ is nominally 10 V but can vary by ± 1 V. Find V_o with no load and with V^+ at its nominal value.

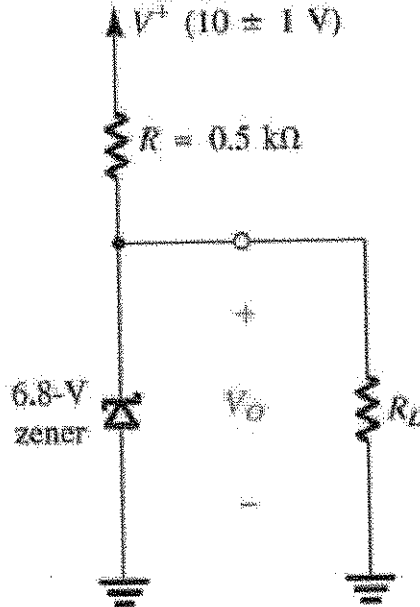


Fig. 3

試題四：〈20分〉

Design the circuit in Fig. 4 to obtain a current I_D of $80\mu A$. Find the value required for R , and find the dc voltage V_D . Let the NMOS transistor have $V_t=0.6$ V, $\mu_n C_{ox}=200\mu A/V^2$, $L=0.8\mu m$, and $W=4\mu m$. Neglect the channel-length modulation effect (i.e., assume $\lambda=0$).

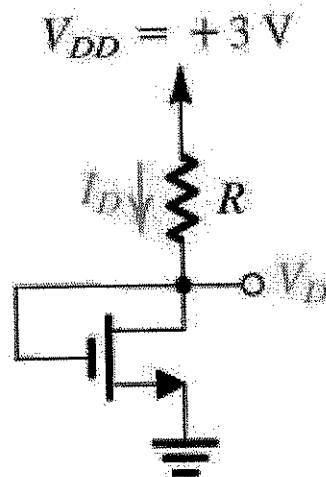


Fig. 4

試題五：〈20分〉

For the circuit shown in Fig. 5, measurement indicates that $V_B = -1.5V$. Assuming $V_{BE} = 0.7V$, calculate V_E , α , β , and V_C . If a transistor with $\beta = \infty$ is used, what values of V_B , V_E , and V_C result?


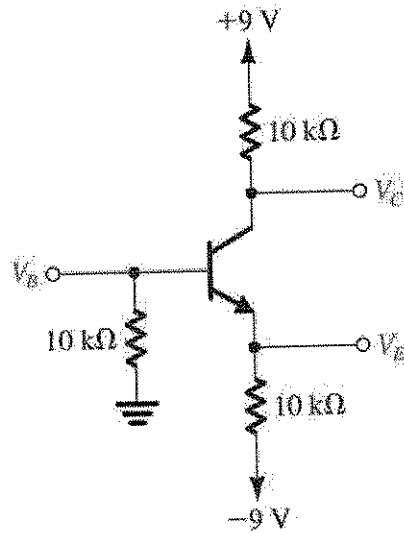


Fig.5

試題六：〈20分〉

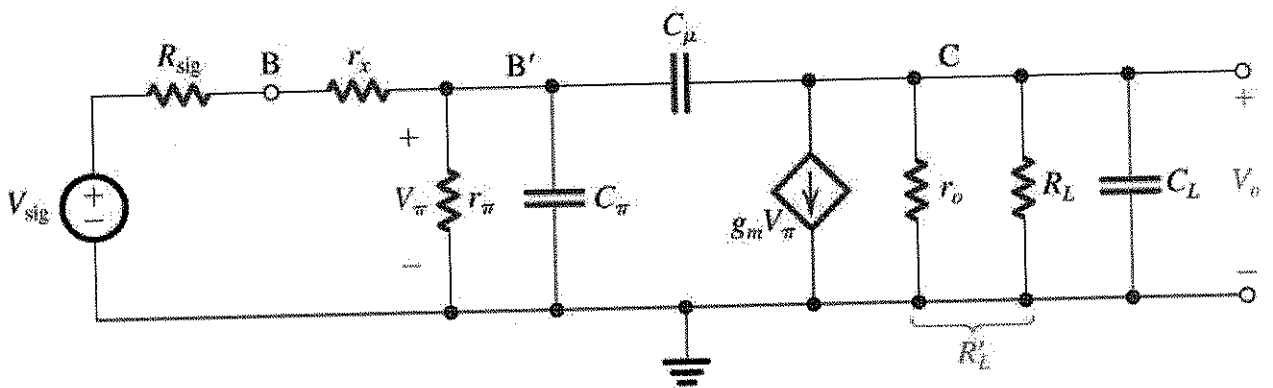A common-emitter amplifier that can be represented by the equivalent circuit of Fig.6 has $C_\pi = 10pF$, $C_\mu = 0.5pF$, $C_L = 2pF$, $g_m = 20mA/V$, $\beta = 100$, $r_x = 200\Omega$, $R'_L = 5k\Omega$, and $R_{sig} = 1k\Omega$. Find the midband gain A_M and an estimate of the 3-dB frequency f_H using the Miller equivalence.



(a)

Fig. 6