

國立勤益科技大學 102 學年度研究所碩士班招生筆試試題卷
 所別：電子工程系碩士班 組別：不分組
 科目：電子學
 准考證號碼： (考生自填)

考生注意事項：

- 一、考試時間 80 分鐘。
- 二、應考人不得自行攜帶電子計算器，一律由本校統一提供。
- 三、

試題一：(20 分)

Find the output voltage of the circuit shown in Fig. 1. (v_o expression in terms of v_1 and v_2)

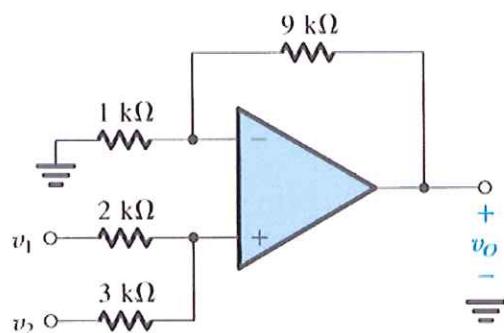


Fig. 1

試題二：(20 分)

Design the circuit in Fig. 2 to obtain a current I_D of 80 μ A. Find the value required for R , and find the dc voltage V_D . Let the NMOS transistor have $V_t=0.6$ V, $\mu_n C_{ox}=200 \mu\text{A/V}^2$, $L=0.8 \mu\text{m}$, and $W=4 \mu\text{m}$. Neglect the channel-length modulation effect (i.e., assume $\lambda=0$)

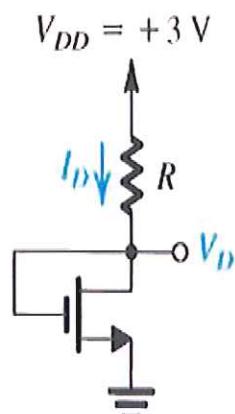


Fig. 2

試題三：(20 分)

Design the circuit in Fig. 3 to establish a drain voltage of 0.1 V. What is the current I_D and R_D ? What is the effective resistance between drain and source at this operating point? Let $V_t=1$ V, $k_n'(W/L)=1$ mA/V², $k_n'=\mu_n C_{ox}$

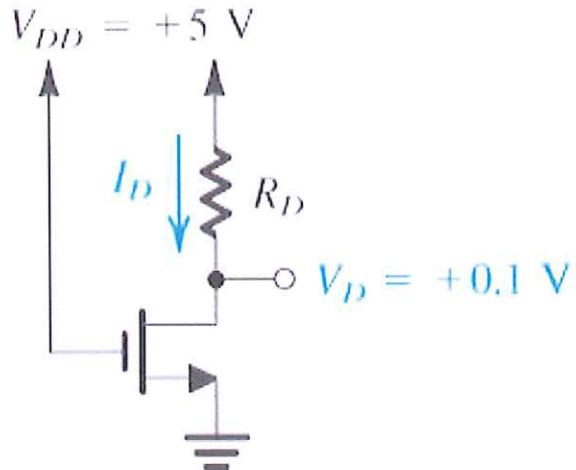


Fig. 3

試題四：(20 分)

We want to analyze the circuit of Fig. 4 to determine I_B , I_C , V_B , and V_C . Assume $\beta=100$, $V_{BE}=0.7$ V.

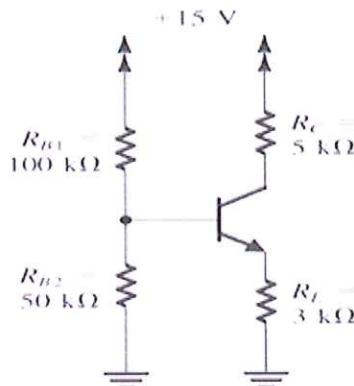


Fig. 4

試題五：(20 分)

Consider the CMOS common-source amplifier in Fig. 5 for the case $V_{DD}=3$ V, $V_m=|V_{tp}|=0.6$ V, $\mu_n C_{ox}=200 \mu\text{A}/\text{V}^2$, and $\mu_p C_{ox}=65 \mu\text{A}/\text{V}^2$. For all transistors, $L=0.4 \mu\text{m}$ and $W=4 \mu\text{m}$. Also Early voltage of $V_{A_n}=20$ V for NMOS, $|V_{A_p}|=10$ V for PMOS, and $I_{REF}=100 \mu\text{A}$. Find the transconductance g_m and the small-signal voltage gain (v_o/v_i) of the common-source amplifier.

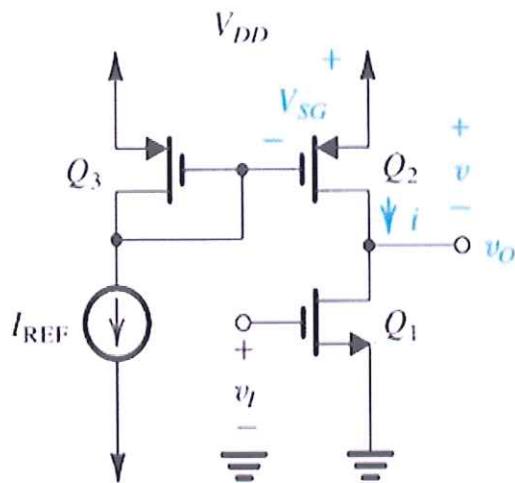


Fig. 5

試題六：〈40 分〉

The transistors in the circuit shown in Fig. 6 have parameters $V_{TND}=V_{TNL}=1\text{V}$, $K_{nD}=50\mu\text{A/V}^2$, and $K_{nL}=10\mu\text{A/V}^2$. Also assume $\lambda_{nD}=\lambda_{nL}=0$. (The subscript D applies to the driver transistor and the subscript L applies to the load transistor.) Find the V_0 for (a) $V_I=5\text{V}$ and (b) $V_I=1.5\text{V}$.

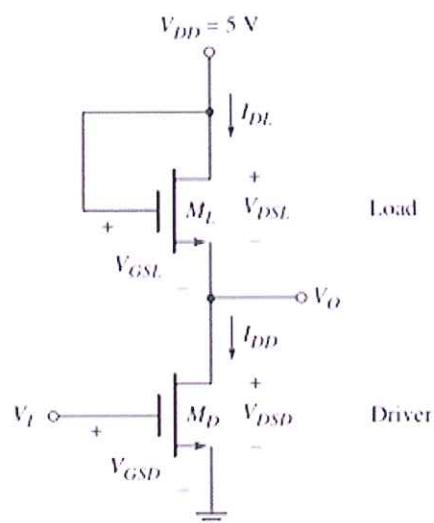


Fig. 6

試題七：〈30分〉

Calculate the small-signal voltage gain of the bipolar transistor circuit shown in Fig. 7. Assume the transistor and circuit parameters are: $\beta=100$, $V_{CC}=12V$, $V_{BE}=0.7V$, $R_C=6k\Omega$, $R_B=50k\Omega$, $V_T=0.026V$ and $V_{BB}=1.2V$.

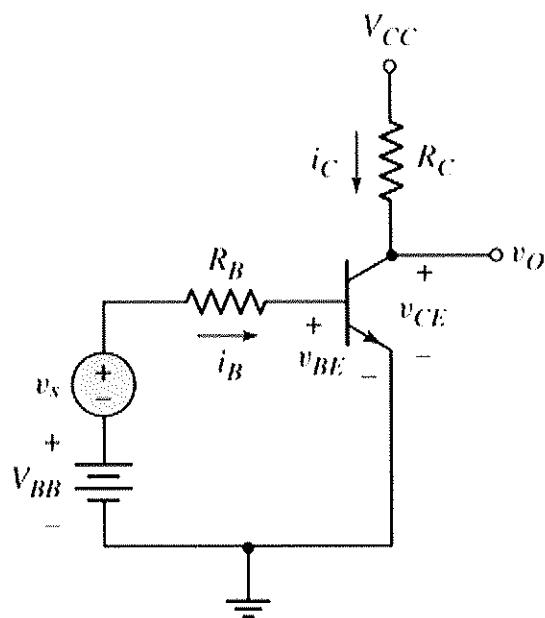


Fig. 7

試題八：〈30分〉

Calculate the differential-mode gain, common-mode gain and common-mode rejection ratio of diff-amp.

Consider the circuit in Fig. 8, with parameters: $V^+=10V$, $V^-=-10V$, $I_Q = 0.8 \text{ mA}$, and $R_C = 12 \text{ k}\Omega$. The transistor parameters are $\beta=100$,

$V_T = 0.026V$ and $V_A = \infty$. Assume the output resistance looking into the constant-current source is $R_o = 25\text{ k}\Omega$. Assume the source resistors R_B are zero.

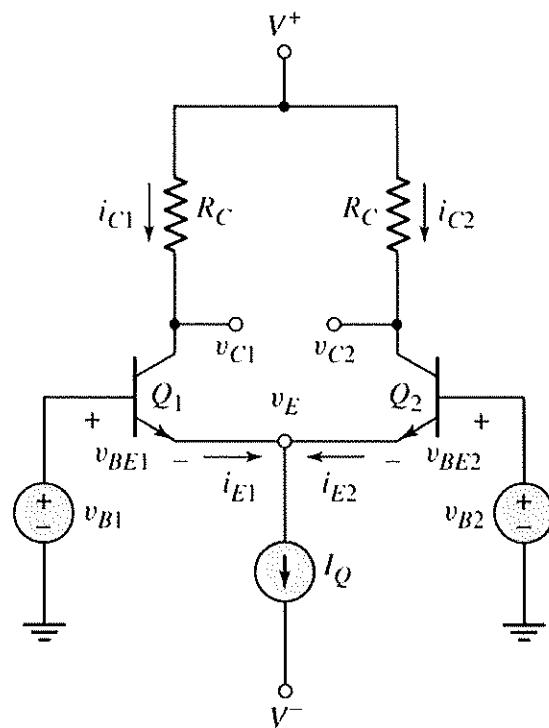


Fig. 8